

Kirchoff's Rules

These are a set of rules to use when analyzing complex / branching circuits. e.g.:

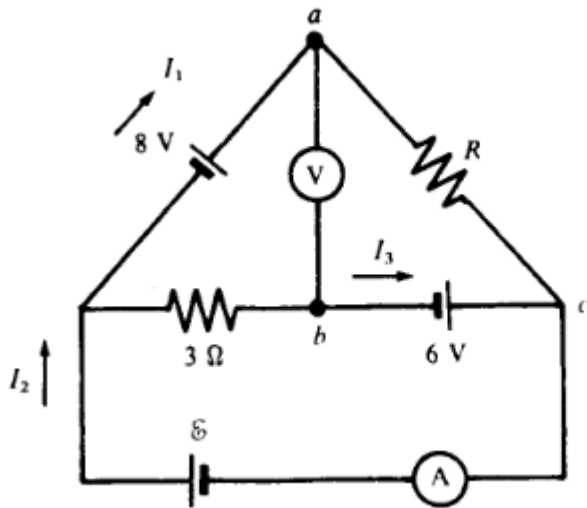


Fig. 27-40

(source: 3000 solved problems in physics fig 27-40 (pg 462))

Junction rule

This rule deals with the current at nodes / branches. Think of the current as the flow of water through a system of rivers. When a series of rivers meet at a junction, the volume of water that goes into the junction is the same as the amount of water that comes out. Same thing with electrical current:

$$\sum_{\text{current flowing in}} I = \sum_{\text{current flowing out}} I$$

Most of the time it's not clear whether current is flowing in or out of a given branch of a junction, so many times the equation looks like this:

$$\sum_{\text{all branches}} I = 0$$

where I is positive if current is flowing in and negative if current is flowing out.

Loop rule

This rule deals with voltage drops around loops in the circuit. Think of these as a roller coaster. Batteries are like chain lifts that lift the train up to a higher potential, and components / resistors are like the drops- bringing the train from a higher gravitational potential to a lower gravitational potential. No matter what, the train finishes at the same elevation that it started at (in other words, the net change in gravitational potential is zero), resulting in:

$$\sum_{loop} V = 0$$

problem solving with kirchoff's loop rules

- each loop / junction will give you an equation
- When using the loop or junction rule, just take a guess as to which way the currents are flowing. If you're wrong about the direction, you'll know because current will be negative
- If there are n components you need to solve for, you will need at least n equations to solve for all of them.

refs:

- [https://phys.libretexts.org/Bookshelves/University_Physics/Book%3A_Calculus-Based_Physics_\(Schnick\)/Volume_B%3A_Electricity_Magnetism_and_Optics/B12%3A_Kirchhoffs_Rules_Terminal_Voltage](https://phys.libretexts.org/Bookshelves/University_Physics/Book%3A_Calculus-Based_Physics_(Schnick)/Volume_B%3A_Electricity_Magnetism_and_Optics/B12%3A_Kirchhoffs_Rules_Terminal_Voltage)